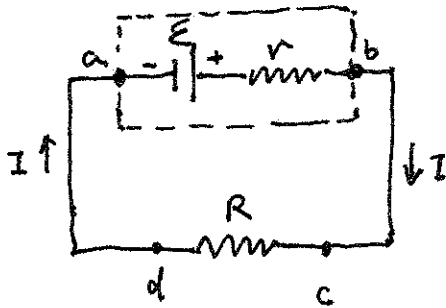


28.1 Electromotive force (EMF)


The EMF of a battery is the maximum possible voltage that a battery can provide.



all battery have internal resistance "r".

$$\Delta V = V_b - V_a = \underbrace{\varepsilon - Ir}_r$$

due to internal resistance r

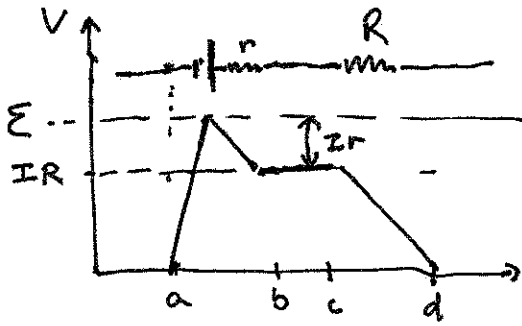

From 28.2b

$$\varepsilon = IR + Ir$$


R ≡ load resistance

$$\rightarrow I = \frac{\varepsilon}{R+r}$$

$$\text{or } I\varepsilon = I^2 R + I^2 r = \text{total power}$$

28.2 Resistans in Series and in parallel

① In series -

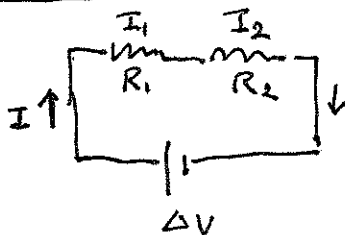


$$I_1 = I_2 = I$$

$$\therefore \Delta V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$\therefore R_{eq} = R_1 + R_2$$

$$\rightarrow R_{eq} = R_1 + R_2 + R_3 + \dots$$

② In parallel

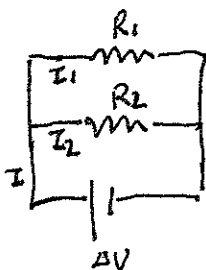

$$I = I_1 + I_2$$

$$= \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \Delta V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\rightarrow \Delta V = I \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$\therefore R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} \text{ or } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

28.3 Kirchhoff's Rules

28-2

When a circuit is not that simple, one can use Kirchhoff's rule to analyze the circuit

1. Junction rule: $\sum I_{in} = \sum I_{out}$

— The sum of current entering any junction is the same as the sum leaving the junction

2. Loop rule:

$$\sum_{\text{closed loop}} \Delta V = 0$$

— Conservation of electric charges

— The sum of potential differences across all elements around any closed loop must be zero


— Conservation of energy

Do example 28.10 multi-loop page 873

28.4 RC Circuit

— Circuit containing Resistor and Capacitor

Changing a Capacitor

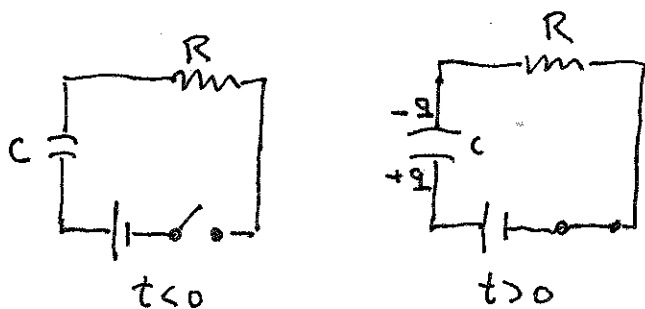

Using Kirchhoff's rule

$$\mathcal{E} - \frac{Q}{C} - IR = 0 \quad (28.11)$$

1) at $t = 0$ (Capacitor is not charged)

$$I_0 = \frac{\mathcal{E}}{R}$$

2) When the capacitor is completely charged, $I = 0$

$$Q = C\mathcal{E}$$

Remember $I = \frac{dq}{dt}$

$$(28.11) \rightarrow \mathcal{E} = \frac{q}{C} - IR = 0$$

$$I = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = -\frac{1}{RC}q + \frac{\mathcal{E}}{R}$$

$$\rightarrow \boxed{\frac{dq(t)}{dt} + \frac{1}{RC}q(t) - \frac{\mathcal{E}}{R} = 0}$$

1st order differential Equation

→ Solution

$$q(t) = C\mathcal{E} (1 - e^{-t/RC})$$

$$= Q (1 - e^{-t/RC})$$

or

$$\frac{dq(t)}{dt} = \frac{C\mathcal{E}}{RC} - \frac{q}{RC}$$

$$= -\frac{q - C\mathcal{E}}{RC}$$

$$\frac{dq(t)}{q - C\mathcal{E}} = -\frac{1}{RC} dt$$



$$\int_0^q \frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = \frac{-t}{RC}$$

$$\rightarrow q(t) = C\mathcal{E} (1 - e^{-t/RC}) = Q (1 - e^{-t/RC}) \quad RC \equiv \tau$$


= time constant
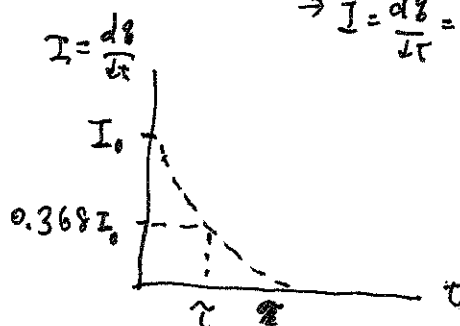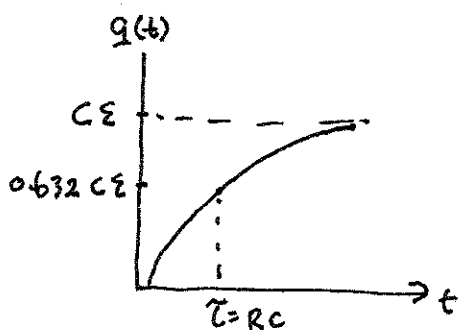
$$\rightarrow I = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$



Note: The dimension of τ

Discharging a Capacitor

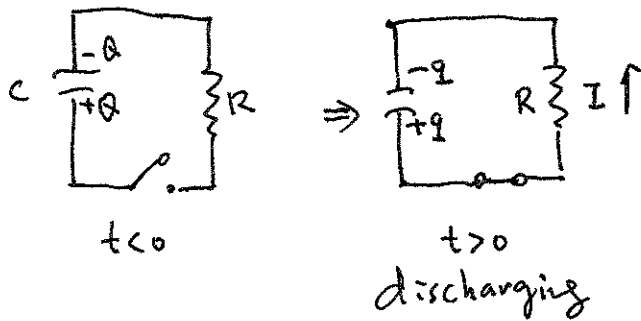

$$-\frac{q}{C} - IR = 0 \quad I = \frac{dq}{dt}$$



$$-R \frac{dq}{dt} = \frac{q}{C} \rightarrow \frac{dq}{q} = -\frac{1}{RC} dt$$

$$\int_Q^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$



$$\rightarrow \ln\left(\frac{q}{Q}\right) = -\frac{t}{RC}$$

$$\rightarrow q(t) = Q e^{-t/RC}$$
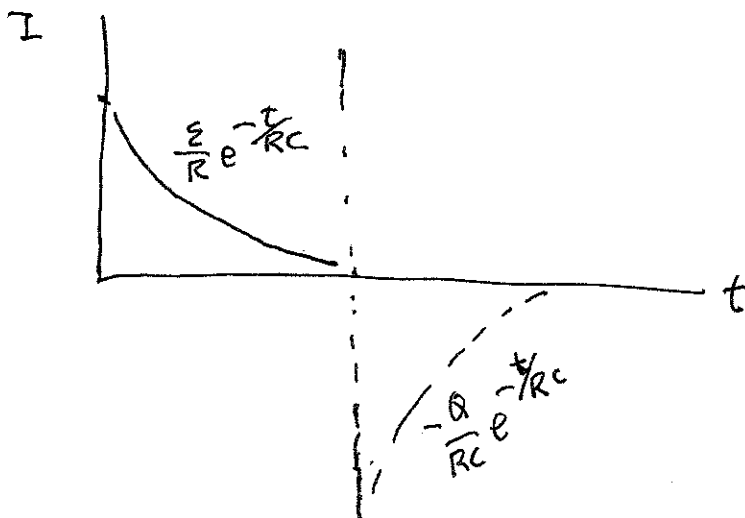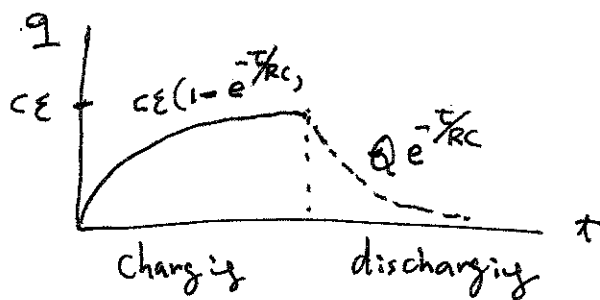
$$\rightarrow I = \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/RC}$$





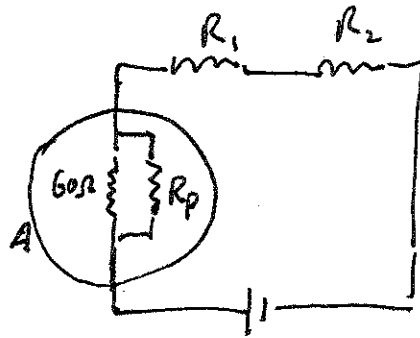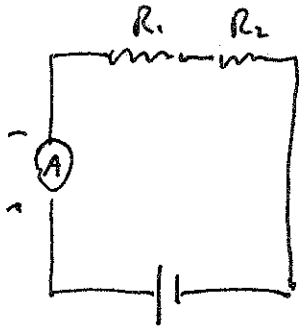The Ammeter : Ideally, an ammeter should have zero resistance, so that the current being measured is not altered.



Connect a R_p : $R_p \ll 60\Omega$ when the galvanometer is used as an ammeter.

The Voltmeter

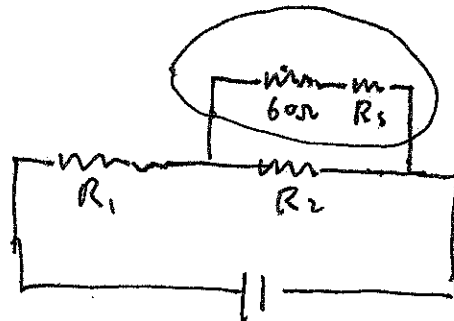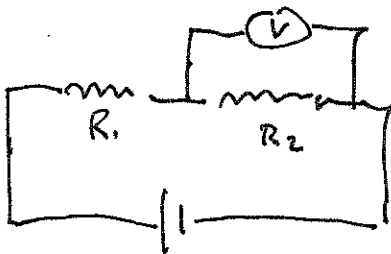

Connect a R_s : $R_s \gg 60\Omega$, when use the galvanometer as a voltmeter.