

SN: _____, Name: _____

Chapter 28-31, Serway; ABSOLUTELY NO CHEATING!

Please write the answers on the blank space or on the back of this paper to save resources.

1.

Label the currents in the branches as shown in the first figure. Reduce the circuit by combining the two parallel resistors as shown in the second figure.

Apply Kirchhoff's loop rule to both loops in Figure (b) to obtain:

$$(2.71R)I_1 + (1.71R)I_2 = 250$$

and $(1.71R)I_1 + (3.71R)I_2 = 500$

With $R = 1\,000\ \Omega$, simultaneous solution of these equations yields:

$$I_1 = 10.0\ \text{mA}$$

and $I_2 = 130.0\ \text{mA}$

From Figure (b), $V_c - V_a = (I_1 + I_2)(1.71R) = 240\ \text{V}$

Thus, from Figure (a), $I_4 = \frac{V_c - V_a}{4R} = \frac{240\ \text{V}}{4\,000\ \Omega} = 60.0\ \text{mA}$

Finally, applying Kirchhoff's point rule at point *A* in Figure (a) gives:

$$I = I_4 - I_1 = 60.0\ \text{mA} - 10.0\ \text{mA} = +50.0\ \text{mA}$$

or $I = \boxed{50.0\ \text{mA from point } A \text{ to point } E}$

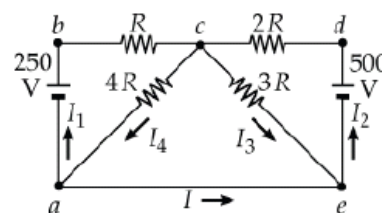


Figure (a)

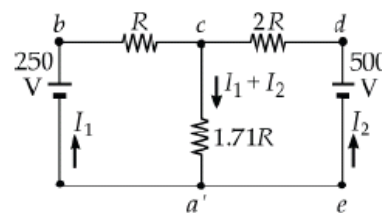


Figure (b)

ANS FIG.1

2.

The emfs induced in the rods are proportional to the lengths of the sections of the rods between the rails. The emfs are $\varepsilon_1 = B\ell v_1$ with positive end downward, and $\varepsilon_2 = B\ell v_2$ with positive end upward, where $\ell = d = 10.0$ cm is the distance between the rails.

Apply Kirchhoff's laws. We assume current I_1 travels downward in the left rod, current I_2 travels upward in the right rod, and current I_3 travels upward in the resistor R_3 .

$$\text{Left loop:} \quad +B\ell v_1 - I_1 R_1 - I_3 R_3 = 0 \quad (1)$$

$$\text{Right loop:} \quad +B\ell v_2 - I_2 R_2 + I_3 R_3 = 0 \quad (2)$$

$$\text{At the top junction: } I_1 = I_2 + I_3 \quad (3)$$

$$\text{Substituting (3) into (1): } B\ell v_1 - I_1 R_1 - I_3 R_3 = 0$$

$$\begin{aligned} B\ell v_1 - (I_2 + I_3) R_1 - I_3 R_3 &= 0 \\ I_2 R_1 + I_3 (R_1 + R_3) &= B\ell v_1 \end{aligned} \quad (4)$$

Use (2) and (4) to solve for I_2 , then equate:

$$\begin{aligned} I_2 &= \frac{B\ell v_2 + I_3 R_3}{R_2} = \frac{B\ell v_1 - I_3 (R_1 + R_3)}{R_1} \\ (B\ell v_2 + I_3 R_3) R_1 &= [B\ell v_1 - I_3 (R_1 + R_3)] R_2 \\ I_3 [R_3 R_1 + (R_1 + R_3) R_2] &= B\ell v_1 R_2 - B\ell v_2 R_1 \\ I_3 &= B\ell \frac{(v_1 R_2 - v_2 R_1)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \\ I_3 &= (0.0100 \text{ T})(0.100 \text{ m}) \frac{[(4.00 \text{ m/s})(15.0 \Omega) - (2.00 \text{ m/s})(10.0 \Omega)]}{(10.0 \Omega)(15.0 \Omega) + (10.0 \Omega)(5.00 \Omega) + (15.0 \Omega)(5.00 \Omega)} \\ &= 1.45 \times 10^{-4} \text{ A} \end{aligned}$$

Therefore, $I_3 = \boxed{145 \mu\text{A upward in the picture}}$, as was originally chosen.