




SN: \_\_\_\_\_, Name: \_\_\_\_\_

Chapter 32-34, Serway; **ABSOLUTELY NO CHEATING!**

**Please write the answers on the blank space or on the back of this paper to save resources.**

- The switch in Figure 1 is connected to position *a* for a long time interval. At  $t = 0$ , the switch is thrown to position *b*. After this time, what are (a) the frequency of oscillation of the *LC* circuit, (b) the maximum charge that appears on the capacitor, (c) the maximum current in the inductor, and (d) the total energy the circuit possesses at  $t = 3.00$  s?

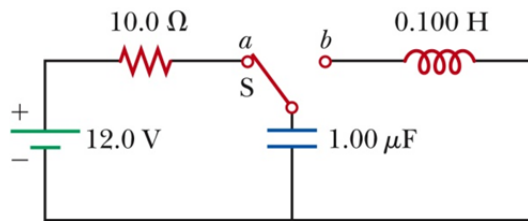

**Figure1**

- A 15.0-mW helium-neon laser emits a beam of circular cross section with a diameter of 2.00 mm. (a) Find the maximum electric field in the beam. (b) What total energy is contained in a 1.00-m length of the beam? (c) Find the momentum carried by a 1.00-m length of the beam.