



Department of Physics
National Dong Hwa University, 1, Sec. 2,
Da Hsueh Rd., Shou-Feng, Hualien, 97401, Taiwan

General Physics-II, Quiz 9
PHYS1000AA, AB, AC: 106-2
2018.06.05

St. ID: _____

Name: _____

*Chapter 26-27, Serway; **ABSOLUTELY NO CHEATING!***

Please write down the answers on the blank space or on the back of this paper. Answer should be in english. [] indicates the question points.

1. Two capacitors, $C_1 = 5.00 \text{ mF}$ and $C_2 = 12.0 \text{ mF}$, are connected in parallel, and the resulting combination is connected to a 9.00 V battery. Find (a) the equivalent capacitance of the combination and the potential difference across each capacitor. (b) What will be the results if they (C_1 & C_2) are connected in series? [25+25= 50]

2. If you want to fabricate a uniform wire from 1.00 g of copper and the wire is to have a resistance of $R = 0.500 \Omega$ and all the copper is to be used, what must be (a) the length and (b) the diameter of this wire ? (c) If the magnitude of the drift velocity of free electrons in this copper wire is $7.84 \times 10^{-4} \text{ m/s}$, what is the electric field in the conductor? [20+10+20=50]