

## General Physics- II, Quiz 10

PHYS10000AA, Fall Semester-107 2019-06-13

Department of Physics National Dong Hwa University, 1, Sec. 2, Da Hsueh Rd., Shou-Feng, Hualien, 97401, Taiwan

St. ID:	Name:
St. 12.	i (dille.

Note: You can use pencil or any pen in answering the problems. Dictionary, calculators and mathematics tables are allowed. Please hand in both solution and this problem sheet.

## ABSOLUTELY NO CHEATING!

## Problems (total 2 problems, 100%)

1. The current in the circuit shown in Figure P32.3 equals 60.0% of the peak current at t = 7.00 ms. What is the lowest source frequency that gives this current. (50%)

Ans: 
$$f = 14.6 \text{ Hz}$$

The current as a function of time is

$$i = \frac{\Delta v}{R} = \left(\frac{\Delta V_{\text{max}}}{R}\right) \sin \omega t.$$

Given the value of *t*, we want to identify a point with

$$0.600 \frac{\Delta V_{\text{max}}}{R} = \frac{\Delta V_{\text{max}}}{R} \sin(\omega t)$$

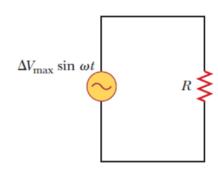


Figure P32.3

Or 
$$\omega t = \sin^{-1} 0.600$$

To find the lowest frequency we choose the smallest angle satisfying this relation:

$$(0.007\ 00\ s)\omega = \sin^{-1}(0.600) = 0.644\ rad$$

Thus, 
$$\omega = 91.9 \text{ rad/s} = 2\pi f$$
 so  $f = 14.6 \text{ Hz}$ 

2. In the AC circuit shown in Figure P32.3, R = 70.0 V and the output voltage of the AC source is  $\Delta V_{\text{max}} \sin \omega t$ . (a) If  $\Delta V_R = 0.250 \Delta V_{\text{max}}$  for the first time at t = 0.010 0 s, what is the angular frequency of the source? (b) What is the next value of t for which  $\Delta V_R = 0.250 \Delta V_{\text{max}}$ ? (50%)

Ans: (a)  $\omega = 25.3 \text{ rad/s}$  (b) t = 0.114 s

(a) From Equation 32.5,  $\Delta v_R = \Delta V_{\text{max}} \sin \omega t$ . To find the angular frequency, we write

$$\Delta v_R = 0.250 (\Delta V_{\text{max}})$$

General Physics II Quiz 9 (107/2018). Dept. of Physics, NDHU.

$$\sin \omega t = 0.250$$

or 
$$\omega t = \sin^{-1}(0.250)$$

The smallest angle for which this is true is  $\omega t = 0.253$  rad. Thus, if t = 0.010 0 s,

$$\omega = \frac{0.253 \text{ rad}}{0.0100 \text{ s}} = \boxed{25.3 \text{ rad/s}}$$

(b) The second time when  $\Delta v_R = 0.250 (\Delta V_{\rm max})$ ,  $\omega t = \sin^{-1}(0.250)$  again. For this occurrence,  $\omega t = \pi - 0.253$  rad = 2.89 rad (to understand why this is true, recall the identity  $\sin(\pi - \theta) = \sin\theta$  from trigonometry). Thus,

$$t = \frac{2.89 \text{ rad}}{25.3 \text{ rad/s}} = \boxed{0.114 \text{ s}}$$