

## 33.1 AC Sources

Time Varying voltage

$$\Delta V = \Delta V_{\max} \sin \omega t$$


$$\omega = 2\pi f = \frac{2\pi}{T}$$

Voltage Amplitude

= generators

= electric outlet

Add a resistor

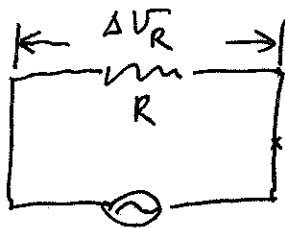

$$\therefore \Delta V = \Delta V_R = \Delta V_{\max} \sin \omega t$$



Instantaneous voltage across the resistor

Instantaneous voltage across the resistor

$$i_R = \frac{\Delta V_R}{R} = \frac{\Delta V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t$$

$$I_{\max} = \frac{\Delta V_{\max}}{R}$$
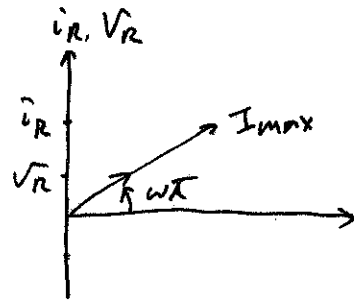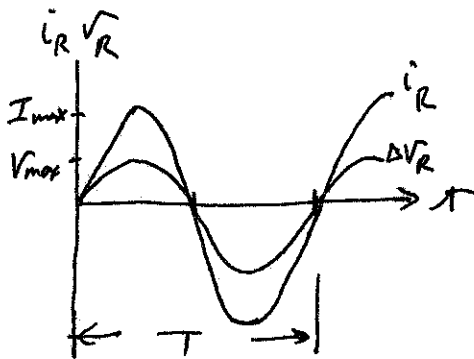
$$\text{or } \Delta V_R = I_{\max} R \sin \omega t$$





Phasor diagram  
→ phasor (A vector)

→ the current in a resistor is always in phase with the applied AC voltage source.

→ the average value of the current over one cycle is zero.

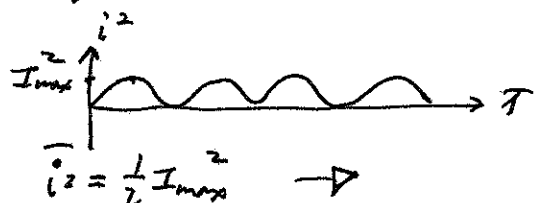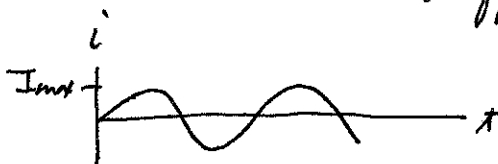Note: the direction of the current does not affect the thermal effect of the resistor.



$$\bar{i^2} = \frac{1}{2} I_{\max}^2 \rightarrow$$

the rate the energy is delivered to a resistor is the power,  $P = i^2 R$

→ the direction of the current does not matter

$$I_{rms} = \sqrt{\overline{i^2}}$$

$$i^2 = I_{max}^2 \sin^2 \omega t$$

$$= \frac{I_{max}}{\sqrt{2}} = 0.707 I_{max}$$

$$\overline{i^2} = \frac{1}{T} \int I_{max}^2 \sin^2 \omega t dt$$

$$= I_{max}^2 \frac{1}{T} \int_0^T \sin^2 \omega t dt$$

$$= \frac{1}{2} I_{max}^2$$

$$P_{av} = I_{rms}^2 R$$

average power delivered to the resistor


$$\frac{1}{T} \int_0^T \sin^2 \omega t dt = \frac{1}{T} \int_0^T \left[ \frac{1 - \sin 2\omega t}{2} \right] dt$$

$$= \frac{1}{2} - \frac{1}{T} \int_0^T \underbrace{\sin \frac{1}{2} \omega t dt}_{=0}$$

$$\Delta V_{rms} = \frac{1}{\sqrt{2}} \Delta V_{max} = 0.707 \Delta V_{max}$$

(Another way of proof) refer to page 1037

② Inductor in an AC current

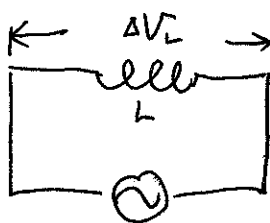

$$\Delta V_L = L \frac{di}{dt} = 0$$



$$\Delta V = L \frac{di}{dt} = \Delta V_{max} \sin \omega t = \Delta V_L$$

$$\frac{di}{dt} = \frac{\Delta V_{max}}{L} \sin \omega t$$

$$di_L = \frac{\Delta V_{max}}{L} \sin \omega t dt$$

$$i_L = \frac{\Delta V_{max}}{L} \int_0^t \sin \omega t dt = -\frac{\Delta V_{max}}{\omega L} \cos \omega t = \left( \frac{\Delta V_{max}}{\omega L} \right) \sin \left( \omega t - \frac{\pi}{2} \right)$$

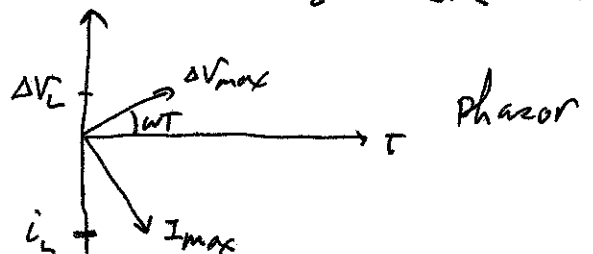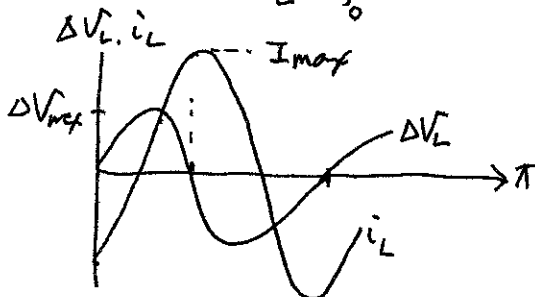∴  $i_L$  and  $\Delta V_L$   $\frac{\pi}{2}$  out of phase



$$i_L = -\frac{\Delta V_{max}}{\omega L} \cos(\omega t) = \frac{\Delta V_{max}}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

- $i_L$  and  $\Delta V_L$  is out of phase by  $\frac{\pi}{2}$
- ~~leads~~ lags the AC by  $\frac{\pi}{2}$

$$I_{max} = \frac{\Delta V_{max}}{\omega L}$$

$$\equiv \frac{\Delta V_{max}}{X_L}$$

$X_L \equiv$  inductive reactance

- has the same unit as resistance

### ③ Capacitor in an AC current


$$\Delta V_C = \Delta V = \Delta V_{max} \sin \omega t$$

$$q = C \Delta V_{max} \sin \omega t$$

$$i_C = \frac{dq}{dt} = \omega C \Delta V_{max} \cos \omega t$$

$$= \omega C \Delta V_{max} \sin(\omega t + \frac{\pi}{2})$$

leads lags the AC by  $\frac{\pi}{2}$

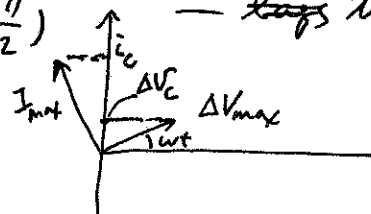

$$I_{max} = \omega C \Delta V_{max}$$

$$= \frac{\Delta V_{max}}{1/\omega C}$$


$$\equiv \frac{\Delta V_{max}}{X_C}$$

$X_C = \frac{1}{\omega C} =$  Capacitive reactance

$$\Delta V_C = \Delta V_{max} \sin \omega t = I_{max} X_C \sin \omega t$$

# ④ The RLC Series Circuit

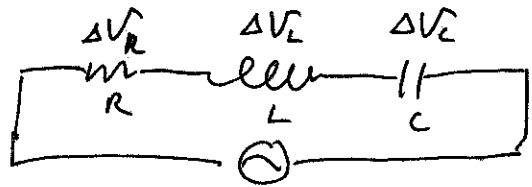1) The current at all points in a Series AC circuit has the same amplitude and phase — for series circuit



$$\Delta V = \Delta V_{max} \sin \omega t$$

$$i = i_{max} \sin(\omega t - \phi)$$

$\phi$  = phase angle

in General: Voltage

R: in phase

L: leads the current by  $\frac{\pi}{2}$

C: lags the current by  $\frac{\pi}{2}$

$$\Delta V = \Delta V_{max} \sin \omega t$$

$$\Delta V_R = I_{max} R \sin \omega t = \Delta V_R \sin \omega t$$

$$\Delta V_L = I_{max} X_L \sin(\omega t + \frac{\pi}{2}) = \Delta V_L \cos \omega t$$

$$\Delta V_C = I_{max} X_C \sin(\omega t - \frac{\pi}{2}) = -\Delta V_C \cos \omega t$$

① in general, the current will not be in phase with that of the AC voltage.


② in general, current will be in same phase

Note: this is the voltage

Also  $\Delta V = \Delta V_R + \Delta V_L + \Delta V_C$

Phasor diagram

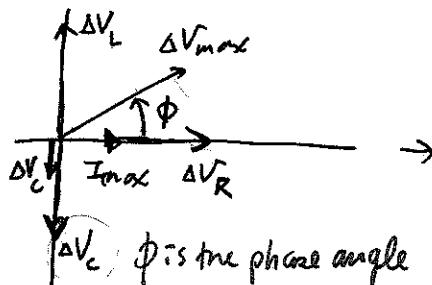(single phasor  $I_{max}$  to represent the current in the elements)



$\phi$  is the phase angle between the current and applied voltage

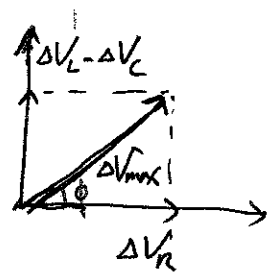


Fig 33.15 (b)


from Fig 33.15 (b) page 1045

$$\Delta V_{max} = \sqrt{\Delta V_R^2 + (\Delta V_L - \Delta V_C)^2}$$

$$= \sqrt{(I_{max} R)^2 + (I_{max} X_L - I_{max} X_C)^2}$$

$$= I_{max} \sqrt{R^2 + (X_L - X_C)^2}$$
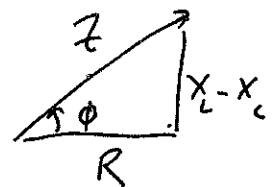
$$\equiv I_{max} Z, \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \text{Impedance } Z \text{ of the circuit}$$



①  $X_L > X_C \rightarrow$  more inductive than capacitive

$X_C > X_L \rightarrow$  more capacitive than inductive

$X_L = X_C \rightarrow$  pure resistive

### 33.6 power in an AC circuit

$$P = i \Delta V = I_{\max} \sin(\omega t - \phi) \Delta V_{\max} \sin \omega t \quad \text{--- for a RLC circuit.}$$

$$= I_{\max} \Delta V_{\max} \sin \omega t \sin(\omega t - \phi)$$

$$= I_{\max} \Delta V_{\max} \sin^2 \omega t \cos \phi \quad \text{But } \sin(\omega t - \phi) = \sin \omega t \cos \phi - \cos \omega t \sin \phi$$

$$- I_{\max} \Delta V_{\max} \underbrace{\sin \omega t \cos \phi}_{\substack{\text{AV} = 0 \\ \text{independent of } t}} \sin \phi$$

$$\sin \omega t \cos \omega t = \frac{1}{2} \sin 2\omega t$$

$$P_{\text{av}} = \bar{P} = \frac{1}{2} I_{\max} \Delta V_{\max} \cos \phi$$

independent of  $t$

$$I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}} \quad (33.4)$$

$$\therefore P_{\text{av}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi$$

power factor

$$\Delta V_{\text{rms}} = \frac{1}{\sqrt{2}} \Delta V_{\max} \quad (33.5)$$

max voltage across the resistor

$$= I_{\max} R$$

$$\rightarrow \cos \phi = \frac{I_{\max} R}{\Delta V_{\max}}$$

$$\therefore P_{\text{av}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi = I_{\text{rms}} \left( \frac{\Delta V_{\max}}{\sqrt{2}} \right) \frac{I_{\max} R}{\Delta V_{\max}} = I_{\text{rms}} \frac{I_{\max} R}{\sqrt{2}}$$

$$P_{\text{av}} = I_{\text{rms}}^2 R, \quad I_{\max} = \sqrt{2} I_{\text{rms}}$$

### 33.7 Resonance in a Series RLC circuit

— A series RLC circuit is said to be in resonance when the current has its maximum value.

$$\text{in general } I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} \quad Z \equiv \sqrt{R^2 + (X_L - X_C)^2} \quad (33.25)$$

$$= \frac{\Delta V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

↑ so the impedance depends on the frequency of the source

Resonance frequency  $\omega$   $X_L - X_C = 0$  ,  $\frac{1}{\omega_0 C} = \omega_0 L$  P33-6

$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$   $\rightarrow$  Also is the same as the natural frequency in a LC circuit

$\rightarrow$  So the current in a series RLC circuit reaches its maximum when the applied voltage matches the natural frequency of the LC components

$\rightarrow$  At resonance, if  $R=0$  then the current becomes infinite

$$P_{av} = I_{rms}^2 R = \frac{(\Delta V_{rms})^2}{Z^2} R = \frac{(\Delta V_{rms})^2 R}{R^2 + (X_L - X_C)^2}$$

$$\text{But } (X_L - X_C)^2 = \left(\omega L - \frac{1}{\omega C}\right)^2 = \frac{L^2}{\omega^2} (\omega^2 - \omega_0^2)^2$$

with  $\omega_0 = \frac{1}{LC}$

$$\therefore P_{av} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$


at resonance,  $\omega = \omega_0$

$$P_{av} = \frac{(\Delta V_{rms})^2}{R}$$

Check page 1050

Fig 33.19

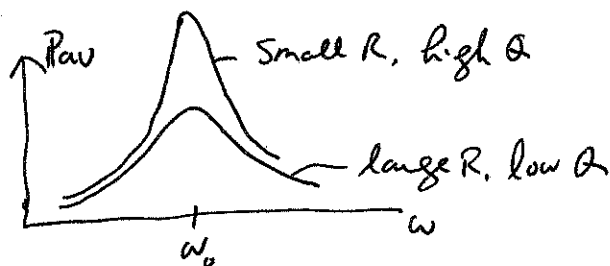
Q-factor = Quality factor =  $\frac{\omega_0}{\Delta \omega}$   $\Delta \omega =$  Full width at half maximum



$\rightarrow$  high Q circuit responds only to very narrow range of the frequency

$\rightarrow$  The tuning of radio receiver

### 33.8 Transformer

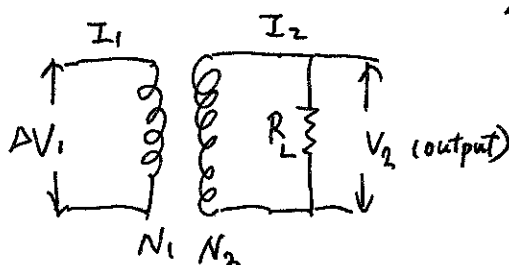

$$\Delta V_1 = -N_1 \frac{d\Phi_B}{dt} \quad , \quad \Delta V_2 = -N_2 \frac{d\Phi}{dt}$$

$$\Delta V_2 = \frac{N_2}{N_1} \Delta V_1 \quad \text{OR} \quad \Delta V_2 N_1 = N_2 \Delta V_1$$

$I_1 \Delta V_1 = I_2 \Delta V_2$  power is the same

Flux is the same in both circuit

$$I_2 = \frac{\Delta V_2}{R_L} \rightarrow I_1 = \frac{\Delta V_1}{R_{eq}} \quad , \quad R_{eq} = \left(\frac{N_1}{N_2}\right)^2 R_L$$

$\Delta V_2 = \frac{N_2}{N_1} \Delta V_1$     (1)  $N_2 > N_1$ , Step up transformer  
 (2)  $N_1 > N_2$ , Step down transformer

$I_2 = \frac{\Delta V_2}{R_L}$      $I_1 = \frac{\Delta V_1}{R_{eq}}$

$\therefore \frac{I_2}{I_1} = \frac{\Delta V_2}{R_L} \frac{R_{eq}}{\Delta V_1} = \frac{\Delta V_2}{\Delta V_1} \frac{R_{eq}}{R_L}$



$\rightarrow R_{eq} = \frac{I_2}{I_1} \frac{\Delta V_1}{\Delta V_2} R_L$     But  $I_1 \Delta V_1 = I_2 \Delta V_2$   
 $\Delta V_2 N_2 = \Delta V_1 N_1$   
 $= \left(\frac{\Delta V_1}{\Delta V_2}\right)^2 R_L$   
 $= \left(\frac{N_1}{N_2}\right)^2 R_L$

33.9 Rectifiers and filters



AC-DC Converter: 120V to 9V  
 Alternating current to DC current.

$\rightarrow$  rectification

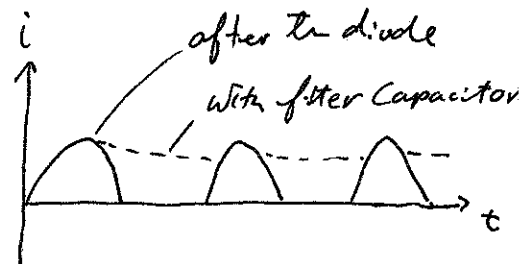
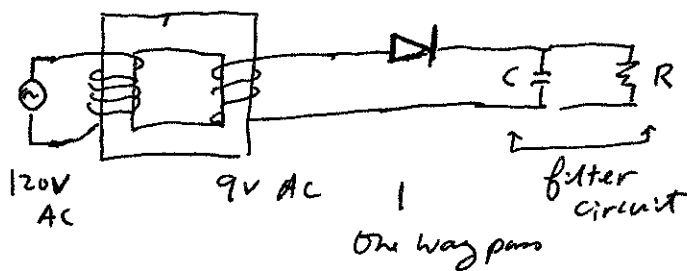
diode: A device element that conduct current in one direction



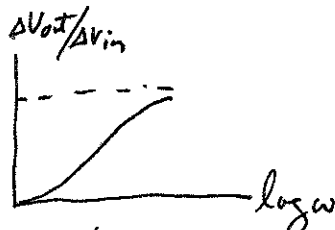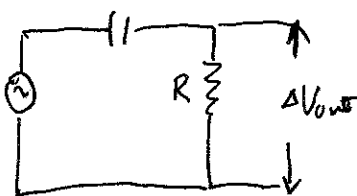RC time constant determines the time varying part of this AC current



high pass filter

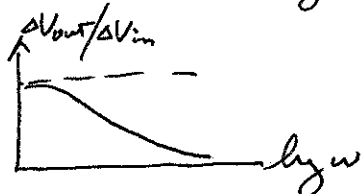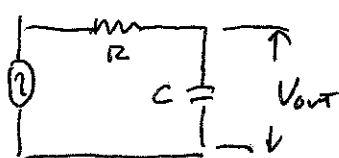

low pass filter