



Solution

1.

(a)

參考答案一、

電磁爐內的「橋式整流器」將一般插座的交流電轉變成直流電，再藉由「功率晶體」將直流電轉變成高週波電流，流經「陶瓷面板」下的「磁熱線圈」。

高週波電流是有規律地改變電流方向，所以由磁熱線圈產生的磁力線就跟著不斷地改變方向，一秒鐘變化二萬次左右，電流方向改變，磁力線的方向也跟著改變。

當鐵質的鍋子放置在這個變動的磁場上，鍋底是受到磁場的感應，產生感應電流，所產生的感應電流又稱為「渦電流」(eddy current)，在鍋底的渦電流，因為金屬導體的電阻關係而產生熱量。

因為電磁爐是以磁感應使炊具產生熱，所以不是所有的鍋子或是器具都適用。要如何選用鍋呢？方法很簡單，只要鍋底能吸住磁鐵的就能用。適合放在電磁爐上的烹飪器具有不鏽鋼鍋、不鏽鋼壺、平底鍋、彩色鍋；不適用的有陶鍋、陶磁壺、『圓底』鐵鍋、耐熱玻璃鍋、鋁鍋、鋁壺。

參考答案二、

原理：

迴路線圈通予電流時，其效果相當於磁鐵棒，因此於線圈面有磁場 N-S 極的產生，亦即有磁通量穿越。假若所使用的電源為交流電，穿越迴路面的磁通量產生變化，當有一鐵性金屬面放置迴路線圈上方金屬面內就會感應電流。

金屬面上有電阻，因此感應的電流會使金屬產生熱量，此熱量用以煮熟食物。感應電流越大，熱量就越高，煮熟食物就越快。要使感應電流越大，穿越金屬面的磁通量變化量要越大，當然磁場要越強，這樣一來原先通予交流電的迴路線圈就要越多匝數纏繞在一起。

構造：

將好幾條長細導線（用漆薄包隔離）合在一起形成相當電纜線，而後依螺旋方彎曲繞成一個大圓蛇餅，兩端接上變壓器。將電磁爐接上家庭用的交流電源(110 伏特)，經變壓器將電壓降低，因此電流增強而輸入電磁爐上的線圈產生高強度的磁場。在煮熟食物的過程中，因為其爐面上沒有電流，所以爐面上溫度不會太高，是一種相對安全的煮食物用器。

(b)

$$\oint_c \vec{E} \cdot d\vec{\ell} = -\frac{d\Phi}{dt} \quad \text{法拉第定律}$$

$$\oint_s \vec{B} \cdot d\vec{s} = \mu_0 I + \mu_0 \epsilon_0 \frac{d\Phi_B}{dt} \quad \text{安培 - 馬克斯定律}$$

$$\oint_s \vec{E} \cdot d\vec{A} = \frac{Q_{in}}{\epsilon_0} \quad \text{高斯定律(電)}$$

$$\oint_s \vec{B} \cdot d\vec{A} = 0 \quad \text{高斯定律(磁)沒有磁單極}$$

2.

2)

(a) Orbital angular momentum.

The circular motion's centrifugal force is provided by the electric force between the electron and the nucleus.

$$\frac{m_e v^2}{r} = \frac{ze^2}{4\pi\epsilon_0 r^2}, \quad z_e = \text{charge of the nucleus}$$

$e = \text{charge of the electron}$

Classically, $L = r \times p = r \times m_e v$, but $r \perp v$.

$$\therefore \vec{L} = m_e v \vec{r}$$

(b) The total classical energy $E = E_K + E_P$.

E_K = The kinetic energy of the electron with velocity.

E_P = The electric potential energy

$$\begin{aligned} \therefore E &= \frac{1}{2} m_e v^2 = \frac{1}{4\pi\epsilon_0} \frac{ze^2}{r} \\ &= \frac{1}{2} \frac{ze^2}{4\pi\epsilon_0 r} - \frac{ze^2}{4\pi\epsilon_0 r} = -\frac{ze^2}{4\pi\epsilon_0 (2r)} \end{aligned}$$

$$\begin{aligned} (c) \quad L &= m_e v r \rightarrow L^2 = m_e (m_e v^2) r^2 = m_e \left(\frac{ze^2}{4\pi\epsilon_0 r} \right) r^2 \\ &= \frac{m_e z e^2 r}{4\pi\epsilon_0} \end{aligned}$$

$$\therefore E = -\frac{ze^2}{4\pi\epsilon_0 (2r)} = -\frac{m_e e^4 z^2}{2(4\pi\epsilon_0)^2 L^2} = -\left(\frac{m_e e^4}{32\pi^2\epsilon_0^2}\right) \frac{z^2}{L^2}$$

(d) If $L = n \hbar$

$$E = -\left(\frac{m_e e^4}{32\pi^2\epsilon_0^2}\right) \frac{z^2}{L^2} = -\left(\frac{m_e e^4}{32\pi^2\epsilon_0^2}\right) \frac{z^2}{n^2 \hbar^2}$$

$$(e) \text{ from (c)} \quad L^2 = \frac{m_e z e^2 r}{4\pi\epsilon_0} = n^2 \hbar^2 \rightarrow r = \frac{(4\pi\epsilon_0) \hbar^2}{z e^2 m_e} n^2 = \left(\frac{a_0}{z}\right) n^2$$

$$a_0 = \frac{(4\pi\epsilon_0) \hbar^2}{e^2 m_e} = 5.29 \times 10^{-11} \text{ m} = 0.5 \text{ \AA}$$

3.

3) When the current through R_5 is zero.

$$\text{then } V_{BC} = 0$$

$$\therefore I_{R_1} = I_{R_3} = I, \quad I_{R_2} = I_{R_4} = I'$$


$$\therefore \Delta V_{AB} = R_1 I, \quad \Delta V_{BD} = R_3 I$$

$$\Delta V_{AC} = R_2 I', \quad \Delta V_{CD} = R_4 I'$$

$$\text{But } \Delta V_{AB} = \Delta V_{AC}, \quad \Delta V_{BD} = \Delta V_{CD}$$

$$\text{or } R_1 I = R_2 I', \quad R_3 I = R_4 I'$$
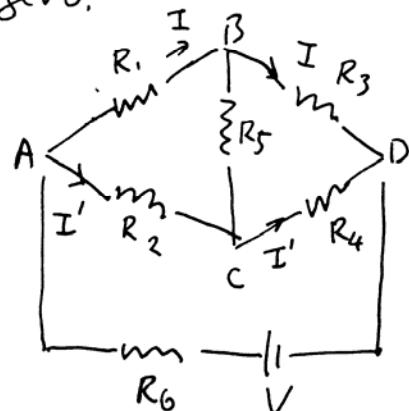
$$\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$



4.

4.

Left-hand loop: $\varepsilon - (I + I_2)R_1 - I_2R_2 = 0$.

Outside loop: $\varepsilon - (I + I_2)R_1 - L \frac{dI}{dt} = 0$.

Eliminating I_2 gives $\varepsilon' - IR' - L \frac{dI}{dt} = 0$.

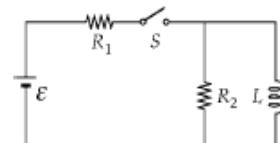


FIG. 4

This is of the same form as Equation 32.6,

so its solution is of the same form as Equation 32.7:

$$I(t) = \frac{\varepsilon'}{R'} \left(1 - e^{-R't/L} \right).$$

$$\text{But } R' = \frac{R_1 R_2}{R_1 + R_2} \text{ and } \varepsilon' = \frac{R_2 \varepsilon}{R_1 + R_2},$$

so

$$\frac{\varepsilon'}{R'} = \frac{\varepsilon R_2 / (R_1 + R_2)}{R_1 R_2 / (R_1 + R_2)} = \frac{\varepsilon}{R_1}.$$

$$\text{Thus } I(t) = \frac{\varepsilon}{R_1} \left(1 - e^{-R_1 t / L} \right).$$

5. Use equation (29.21) in the text book

$$\text{P29.39} \quad B = \frac{nqt(\Delta V_H)}{I} = \frac{(8.46 \times 10^{28} \text{ m}^{-3})(1.60 \times 10^{-19} \text{ C})(5.00 \times 10^{-3} \text{ m})(5.10 \times 10^{-12} \text{ V})}{8.00 \text{ A}}$$

$$B = 4.31 \times 10^{-5} \text{ T} = 43.1 \mu\text{T}$$